

-: National Institute of Technology
Surathkal, Karnataka....:-

Lab Assignment: 3

Name:- Chikkari Chinnappa.

Roll No:- 211IT017

Topic:- IT110 - Digital System
Design.

① SR Flip-Flop to JK Flip-flop Conversion.

J and K will be given as External inputs to S and R. As shown in logic diagram below. S and R will be the outputs of the Combinational Circuit.


J-K Inputs		Outputs		S-R Inputs	
J	K	Qp	Qp+1	S	R
0	0	0	0	0	X
0	0	1	1	X	0
0	1	0	0	0	X
0	1	1	0	0	1
1	0	0	1	1	0
1	0	1	1	X	0
1	1	0	1	0	1
1	1	1	0	1	1


The Truth table for the Flip flop conversion are given below. The present state is denoted by Qp and Qp+1 is the Next State to be obtained when the J and K inputs are Applied.

J	Kp			
	0	1	3	2
0	0 ⁰	X ¹	0 ³	0 ²
1	1 ⁴	X ⁵	0 ⁷	1 ⁶

J	Kp			
	0	1	3	2
0	X ⁰	0 ¹	1 ³	X ²
1	0 ⁴	0 ⁵	1 ⁷	0 ⁶

For two inputs J and K , there will be eight possible combinations. For each combination for each combination of J , K and Q_p , the corresponding Q_{p+1} states are found. Q_{p+1} simply suggests the future values to be obtained by the JK Flip Flop after the value of Q_p . The table is then completed by writing the values of S and R required to get each Q_{p+1} from the corresponding Q_p . That is, the values of S and R that required to change the state of the flip flop from Q_p to Q_{p+1} are written.

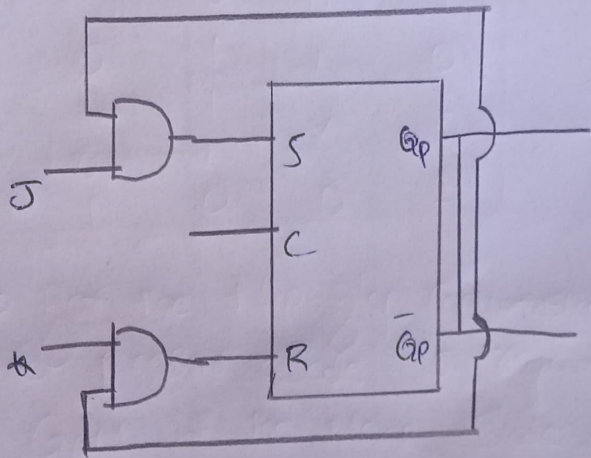

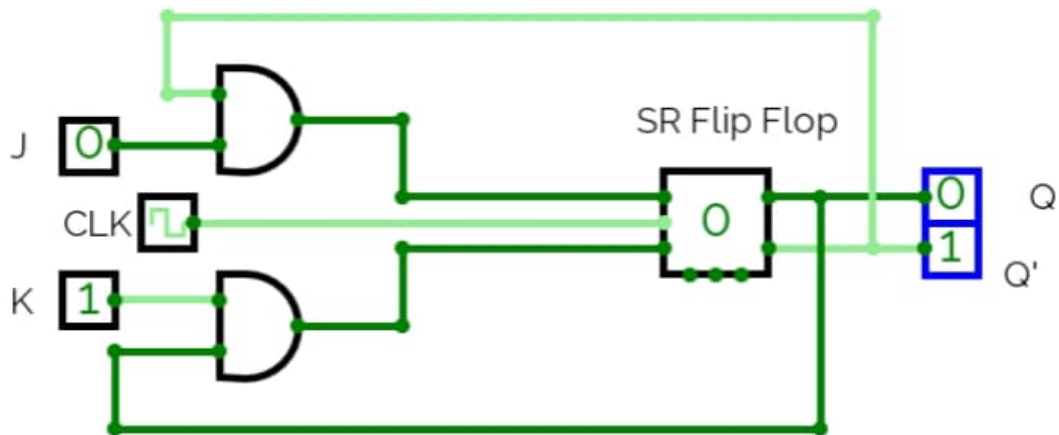

② JK Flip-flop to D Flip-flop Conversion.

By writing the JK-to-D conversion let use a K-map to Obtain Logic Expressions for the Inputs for J & K. in terms of D & Q.

It can be seen that given Jk flip flop can be converted into a D-type flip flop by driving J & K inputs pins with the D input & its Negation. Respectively. Thus the additional hardware components required would be a NOT gate. Resulting the Digital System.

D Inputs	Outputs		J-K Inputs	
	Q _P	Q _{PA}	J	K
0	0	0	0	X
0	1	0	X	1
1	0	1	1	X
1	1	0	X	0

We shall verify our system so as to ensure that it behaves like we expect.


It can be clearly seen that the entries in the first, second, & sixth columns of the JK-to-D reorganization table (shaded in beige) are the same as those in the D Flip-flop Truth Table. Thus, it can be concluded that the conversion process of JK flip-flop into D-type.

D \ Q	Q	
	0	1
0	0	X
1	1	X

$J = D$

D \ Q	Q	
	0	1
0	X	1
1	X	3

$K = \bar{D}$

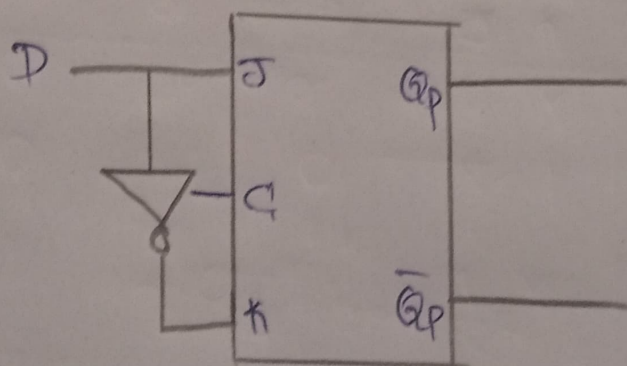

JK FLIP FLOP USING D FLIP FLOP

