

Format of Lab Exam **IT110**

40 Marks - 2 hrs

1.

a. Minimization Using K-Map (7 marks)

- Writing Expression minimization each step using K map (5 marks)
- Circuit Verse simulation (2 marks)

b. Flip Flop Conversion (6 marks)

- Write up as written in your assignment
- Each truth table , Conversion table, Excitation table, verification table
- Circuit verse implementation

2. Code Converter (10 marks)

- Write up as written in your assignment with each reduction steps (4 marks)
- Truth Table (3 marks)
- Circuit verse implementation (3 marks)

3. HDL Program (7 marks)

- Writing the program and execute in eda (5 marks)
- Clock waves (2 marks)

4. Counters OR PLA (Any 1) (10 marks)

- Write up as written in your assignment with each reduction steps (4 marks)
- Truth Table (3 marks)
- Circuit verse implementation (3 marks)